# IITB-RISC

Project 1

Multi-Cycle Implementation

OV Shashank; Avineil Jain; Pratik Brahma; Yogesh Mahajan GROUP NUMBER : 16

# **CONTENTS**

Microprocessor Design	2
State Elaboration	2
State Flow Diagram	3
Datapath Design	5
Instruction Set	6
Instructions that affect Flag Settings	6
Instruction Set and Addressing Modes	6
Instruction Encoding	6
Instruction Timing Reference	7
Custom Instructions	7
VHDL Codes	8
Components	8
Microprocessor Blocks	8
Testing	8
Assembler	8
Bootloader-Software	8
Quartus Project	9
Bootloader (Edits to support the bootloader)	9
Miscellaneous	10
Team Members	10
Problems Faced	10
Interesting Aspects	10
Testing Procedure	10

# MICROPROCESSOR DESIGN


(Does not include the bootload states)


## STATE ELABORATION

SIAIL	LLABONATION
S1	$R7 \rightarrow MEM (A)$ $MEM (D) \rightarrow IR$ $R7 \rightarrow ALU$ $+1 \rightarrow ALU$ $ALU \rightarrow PC$
S2	$\begin{array}{c} I_{6-8} \rightarrow A1_{RF} \\ I_{9-11} \rightarrow A2_{RF} \\ D1 \rightarrow E1 \\ D2 \rightarrow E2,T1 \\ I_{0-7} \rightarrow PE_{INPUT} \end{array}$
\$3	E1 → ALU E2 → ALU ALU → T1
S4	$I_{3-5}/I_{6-8} \rightarrow A3_{RF}$ $T1 \rightarrow D3_{RF}$
S5	$PC \rightarrow D3_{RF}$ "111" \rightarrow A3_{RF} $T2 \rightarrow ALU$ $0 \rightarrow ALU$
S6	$I_{0-8} \rightarrow SE_{9-16} \rightarrow LS_7$ $LS_7 \rightarrow D3_{RF}$ $I_{9-11} \rightarrow A3_{RF}$
S7	E1 $\rightarrow$ ALU $I_{0-5} \rightarrow SE_{6-16} \rightarrow ALU$ ALU $\rightarrow$ T1 , MEM(A)
\$8	MEM (DO) $\rightarrow$ T2, D3 <sub>RF</sub> $I_{9-11} \rightarrow A3_{RF}$

S9	D2 $\rightarrow$ MEM <sub>10</sub> (DI) PC $\rightarrow$ D3 <sub>RF</sub> "111" $\rightarrow$ A3 <sub>RF</sub>
S10	do { MEM <sub>DAT</sub> (DO) → T2}
S11	$T2 \rightarrow D3_{RF}$ $PE_{OUTPUT} \rightarrow A3_{RF}$ $T1 \rightarrow ALU$ $+1 \rightarrow ALU$ $ALU \rightarrow T1,MEM(DI)$ } while (! invalid_next);
S12	$PE_{OUTPUT} \rightarrow A2_{RF}$ $T1 \rightarrow MEM(A)$
S13	$T1 \rightarrow ALU$ $+1 \rightarrow ALU$ $ALU \rightarrow T1$ while (! invalid_next);
S14	$R7 \rightarrow ALU$ $I_{0-5} \rightarrow SE_{6-16} \rightarrow ALU$ $ALU \rightarrow PC$
S15	$PC \rightarrow D3_{RF}$ $I_{9-11} \rightarrow A3_{RF}$ $R7 \rightarrow ALU$ $I_{0-8} \rightarrow SE_{9-16} \rightarrow ALU$ $ALU \rightarrow PC$
S16	$D1_{RF} \rightarrow PC$ $I_{9-11} \rightarrow A3_{RF}$ $PC \rightarrow D3_{RF}$


## STATE FLOW DIAGRAM

 

 
 
## DATAPATH DESIGN

(Does not reflect the presence of the bootloader block)



# **INSTRUCTION SET**

IITB - RISC

# **INSTRUCTION SET**

## INSTRUCTIONS THAT AFFECT FLAG SETTINGS

Instruction	Flags		Instruction	Flags			
	С	Z	OV		C	Z	OV
ADD	Х	Χ	Х	NDU		Х	
ADC	Х	Х	Х	NDC		Х	
ADZ	Х	Х	Х	NDZ		Х	
ADO	Х	Х	Х	NDO		Х	
ADI	Х	Х	Х	LW		Х	

### INSTRUCTION SET AND ADDRESSING MODES

R <sub>n</sub>	Registers R6-R0 of the Register Bank			
data 6	Signed 6-bit constant included in instruction			
data 9	Signed 9-bit constant included in instruction			
rel 6	Signed (two's complement) 6-bit offset byte. Used by BEQ. Range is -32 to +31			
	short words relative to the present instruction			
rel 9	Signed (two's complement) 9-bit offset byte. Used by JAL. Range is -256 to +255			
	short words relative to the present instruction			
reg	8-bits representing registers R7-R0. Used by LM and SM			
R <sub>7</sub>	Program Counter			
R	Registers R7-R0 of the Register Bank			

## INSTRUCTION ENCODING

ADD:	00_00	RA	RB	RC	0	00	
ADC:	00_00	RA	RB	RC	0	10	
ADZ:	00_00	RA	RB	RC	0	01	
ADO:	00_00	RA	RB	RC	0	11	
ADI:	00_01	RA	RB	RB data 6			
NDU:	00_10	RA	RB	RC	0	00	
NDC:	00_10	RA	RB	RC	0	10	
NDZ:	00_10	RA	RB	RC	0	01	
NDO:	00_10	RA	RB	RC	0	11	
LHI:	00_11	RA	data 9				
LW:	01_00	RA	RB rel 6				
SW:	01_01	RA	RB rel 6				
LM:	01_10	RA	reg				
SM:	01_11	RA	reg				
LLI:	10_11	RA	data 9				
BEQ:	11_00	RA	RB rel 6				
JAL:	10_00	RA	rel 9				
JLR:	10_01	RA	RB 000_000				

# **INSTRUCTION SET**

IITB - RISC

#### INSTRUCTION TIMING REFERENCE

INSTRU	JCHON I	IIVIII	NG KI	<u>:FER</u>	ENCE			
Mne	emonic	Flags C Z OV		OV	Oscillator Period		N	1nem
ADD	R <sub>n</sub> , R, R	Х	X	Х	5		ADI	R <sub>n,</sub> F
ADD	R <sub>7</sub> , R, R	Х	Х	Х	4		ADI	R <sub>7,</sub> F
ADC	R <sub>n</sub> , R, R	0	Х	Х	5		LHI	R <sub>n</sub> ,
ADC	R <sub>7</sub> , R, R	0	Х	Х	4		LHI	R <sub>7</sub> ,
ADC	R <sub>n</sub> , R, R	1	Х	Х	3		LLI	R <sub>n</sub> ,
ADZ	R <sub>n</sub> , R, R	Х	0	Х	5		LLI	R <sub>7</sub> ,
ADZ	R <sub>7</sub> , R, R	Х	0	Х	4		LW	R,
ADZ	R <sub>n</sub> , R, R	Х	1	Χ	3		SW	R,
ADO	R <sub>n</sub> , R, R	Х	Х	0	5		LM	F
ADO	R <sub>7</sub> , R, R	Х	Х	0	4		SM	F
ADO	R <sub>n</sub> , R, R	Х	Х	1	3		JAL	R
NDU	R <sub>n</sub> , R, R	Х	Х	Χ	5		JAL	R
NDU	R <sub>n</sub> , R, R	Х	Х	Х	4		JLR	
NDC	R <sub>n</sub> , R, R	0	Х	Х	5		JLR	
NDC	R <sub>7</sub> , R, R	0	Х	Х	4		BEQ	
NDC	R <sub>n</sub> , R, R	1	Х	Х	3		BEQ	
NDZ	R <sub>n</sub> , R, R	Х	0	Х	5			
NDZ	R <sub>7</sub> , R, R	Х	0	Х	4			
NDZ	R <sub>n</sub> , R, R	Х	1	Х	3			
NDO	R <sub>n</sub> , R, R	Х	Х	0	5			
NDO	R <sub>7</sub> , R, R	Х	Χ	0	4			
NDO	R <sub>n</sub> , R, R	Х	Х	1	3			

Mnemonic		Flags/ Condition	Oscillator Period
ADI	R <sub>n,</sub> R, data6	Х	5
ADI	R <sub>7,</sub> R, data6	Х	4
LHI	R <sub>n</sub> , data9	Х	3
LHI	R <sub>7</sub> , data9	Х	2
LLI	R <sub>n</sub> , data9	Х	3
LLI	R <sub>7</sub> , data9	Х	2
LW	R, R, rel6	Х	5
SW	R, R, rel6	Х	4
LM	R, reg	Х	3+2*reg_count
SM	R, reg	X	3+2*reg_count
JAL	R <sub>n</sub> , rel9	Χ	3
JAL	R <sub>7</sub> , rel9	Х	2
JLR	R <sub>n</sub> , R	Χ	3
JLR	R <sub>7</sub> , R	Х	2
BEQ		Not Equal	3
BEQ		Equal	4

#### **CUSTOM INSTRUCTIONS**

- ADO: ADD if the overflow flag is set. The rest of the instruction format is the same as the other conditional execution instructions
- NDO: NAND if the overflow flag is set. The rest of the instruction format is the same as the other conditional execution instructions
- LLI: Load lower immediate. Load the immediate 9 bits into the register as mentioned in the instruction without sign extension by padding zeros in the upper 7 bits.

NOTE: The microprocessor is supposed to be a signed microprocessor and hence the overflow bit was introduced. It may be considered as the signed equivalent of the carry bit. The carry bit here still represents the unsigned version and hence the two must be used carefully.



IITB - RISC

#### VHDL CODES

(All the codes have been hyperlinked here for easy viewing; Notepad++ or gedit is recommended)

#### **COMPONENTS**

- ALU
- Priority Encoder
- Load/Store Multiple Logic Block
- Registers
- Memory (Generated using Altera's MegaWizard Takes no HEX Input File Use Bootloader)
- Register File
- Sign Extender

#### MICROPROCESSOR BLOCKS

- <u>Data Path</u>: This consists of the entire data path along with all the transfers and the
  predicates corresponding to an RTL layout of the microprocessor. All the T and S signals are
  pretty accurately detailed as comments at the beginning of the architecture.
- <u>Control Path</u>: This consists of the controller Moore FSM. It has been decomposed into three processes; The first one describes the flip flops which control the states, the second one describes the next state logic and finally the third process controls the output logic based on the present state. (The order in the code might not exactly follow this order). All the T signals have been accompanied by the expected result they are to cause in the data path.
- <u>IITB\_RISC</u>: The top-level entity than combines the data path and the controller FSM. The register 0 has been shown as an output so that the processes of the microprocessor can be displayed outside in hardware.
- <u>Bootloader</u>: The bootloader block. More information can be found <u>here</u>.

#### **TESTING**

• <u>Test\_final</u>: This is a test bench which can be used to simulate the entire microprocessor in Altera's modelsim. It basically functions to provide the clock and reset signals to the microprocessor.

Testing results have been stored as images and are also available along with this document.

#### **ASSEMBLER**

The code <u>assembler.py</u> was developed as a combined effort of Kalpesh and Shashank. It basically works by taking as its input a text file containing code written in an assembly like language, and creates an INTEL HEX file which can be directly provided to Quartus which uses it to preload memory. A <u>sample hex</u> file produced by the code is provided along with this document. Also, a <u>sample text</u> input file has also been included. More information on the syntax can be found <u>here</u>.

#### **BOOTLOADER-SOFTWARE**

The code <u>serial\_boot.py</u> can be used in conjunction with the bootloader hardware as described in the <u>README</u> to program the microprocessor memory to contain any set of instructions. More information on its utilisation can be found <u>here</u>.

# **CODES**


#### IITB - RISC

#### **QUARTUS PROJECT**

The <u>quartus project folder</u> used for testing is also included along with this submission. This can be used for quick compilation and viewing in Quartus. Necessary settings have been implemented to allow for timing analysis and RTL and gate level simulation. The bootloader has been integrated into the design.

 
### Pin Mapping:


- Last 8 Bits of the Register R0 have been mapped to the LEDs. It can be used to see visible results.
- KEY [0] is the RESET Button. It is active LOW.
- KEY [1] is the BOOTLOAD Button. It is too active LOW.
- GPIO\_00 is the UART RX Pin.



To send into bootloader mode, while keeping the Boot Key pressed, press and release the Reset Button and then release the Boot Key. The microprocessor enters the boot mode.
 
### BOOTLOADER (EDITS TO SUPPORT THE BOOTLOADER)



 

# **CODES**

#### IITB - RISC

## **MISCELLANEOUS**

#### **TEAM MEMBERS**

- 1. Avineil Jain
- 2. Pratik Brahma
- 3. Yogesh Mahajan
- 4. OV Shashank

#### PROBLEMS FACED

- Minor Bugs in code leading to improper execution of instructions
- Dealing with delays due to input registers present in the Altera MegaWizard Generated RAM
- Behavioural to Synthesisable: Only change that was needed was to replace the memory. Everything else had been taken care of from the beginning itself.
- As such did not find anything challenging

#### **INTERESTING ASPECTS**

- Having the microprocessor run on the FPGA
- Running the Bootloader successfully
- Creating this document...

#### **TESTING PROCEDURE**

- GHDL Simulation
- Gate Level Simulation of all instructions
- On FPGA: Ran a code that started a counter on RO with variable delay times. The delay times could be measured and were pretty accurate.